
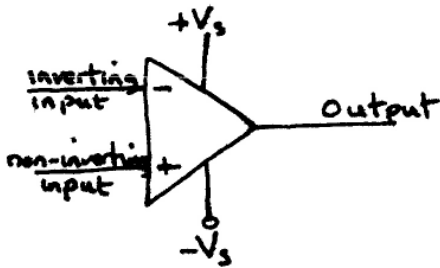


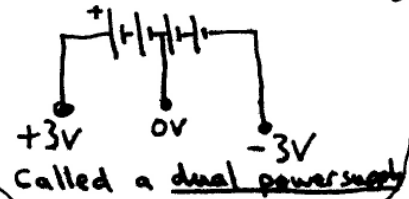1.4 Operational Amplifiers (worth 30% of marks → Chapter 9).



What does it do? Amplifies difference between the voltages at + and - input. (A voltage amplifier)


Power supply (p8) needs +Vs and -Vs eg. +15V and -15V to work. 0Volts is halfway between the two.



Voltage of output (p9)

- Output is positive when + is higher than -
- Output is zero when + = -
- Output is negative when - is higher than +.

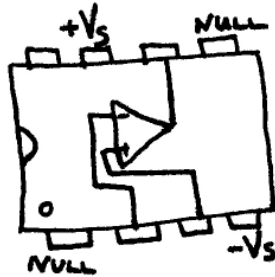The 741 is (p8) an 8 pin DIL chip with an op-amp on it



Open loop gain (p4)

Gain means 'how many times the signal is amplified'. A gain of 10 would mean output is 10 times bigger than input.

Open loop gain is called A₀

$$A_0 = \frac{V_{out}}{V_{in}}$$

Properties of an Op-Amp (p11)


1. Very high open loop gain (A₀)
 - Ideally infinite
 - Actually about 100,000
2. Very high input impedance so that it takes only a very tiny current from input signal
 - Ideally infinite - no current taken.
 - Actually a few MΩ
 - ↑ mega (million)
3. Very low output impedance so it can deliver a big current
 - Ideal: zero
 - Actual ~ 100Ω
4. Very wide bandwidth so it can amplify low and very high frequency signals well.
 - Ideal: infinite bandwidth
 - Actual: a few kHz.
 - ↑ Kilo = 1000

1.4 Operational Amplifier - (continued)

High gain doesn't mean massive output voltage!!


A gain of 10,000 and a difference in V_+ and V_- of 0.1V should mean an output of $0.1 \times 10,000$ or 1,000 Volts. This is impossible because the output cannot be higher than the supply voltage. In practice it only goes up to about 85% of the supply voltage.

This is called saturation see (p10)

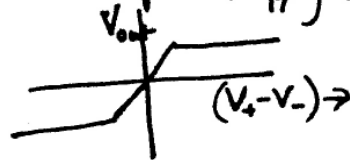

(p6)

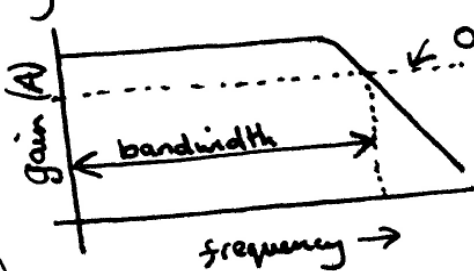Bandwidth - If the frequency of the input increases, the gain should stay the same for the output. However, eventually the gain drops.



Look for where the gain drops to 0.7 of its maximum value. The frequency of this point is the bandwidth.

Slew rate (p6)

The output takes a while to increase or decrease its voltage. Slew rate is the maximum rate of change of output voltage.

Slew rate = $10V/\mu s$
 \uparrow micro (millionth)


It takes $2\mu s$ to change by 20V.

Gain-Bandwidth Product (p7)


Gain \times bandwidth = constant.
 So increasing gain will decrease bandwidth + vice versa

Offset Null (p9)

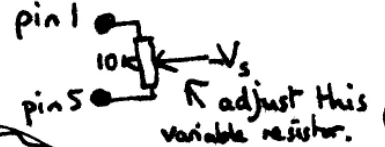IF $V_+ = V_-$ the output should also be 0V. However sometimes an adjustment has to be made so that it is actually zero. pin 1 and 5 make this possible



Amplifiers in Series

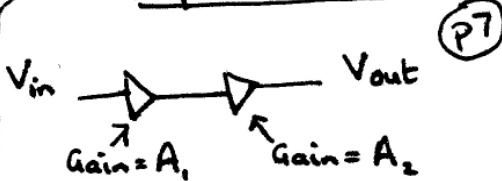

Total gain = $A_1 \times A_2$

Feedback

Sending part of output back into input.


Effect: reduces Gain (A)

1.4 Operational Amplifier - ctd

2 practical circuits Inverting Amplifier and Non Inverting Amplifier

Both circuits → resistors are added to give negative feedback to reduce the gain (A). This makes the amplifier more stable.



Inverting Voltage Amplifier

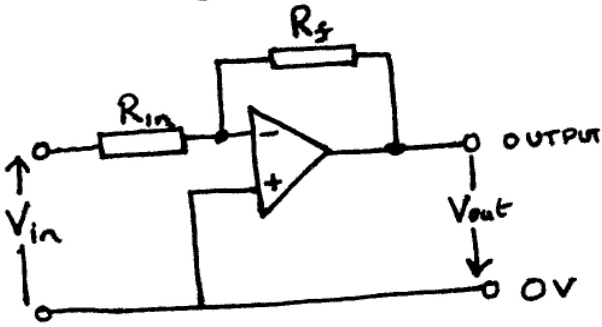

$$\text{Gain (A)} = -\frac{R_f}{R_{in}}$$


The output is amplified and inverted

Input impedance is R_{in}

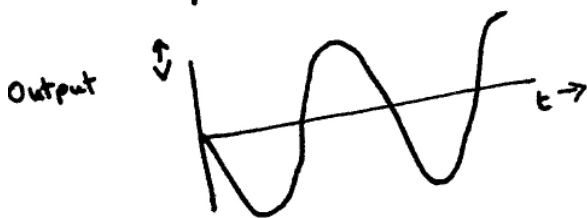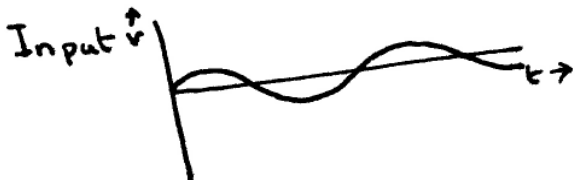

Note: output is inverted and amplified

Non-inverting voltage amplifier

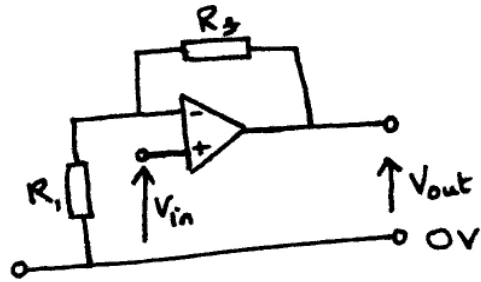

$$\text{Gain (A)} = 1 + \frac{R_f}{R_1}$$

The output is amplified but not inverted.

Input impedance is the same as op-amp.




Output is amplified but not inverted

Clipping The output can only go up to the saturation voltage.

What happens if it goes higher → it can't so stays at saturation voltage.

If output should be this.

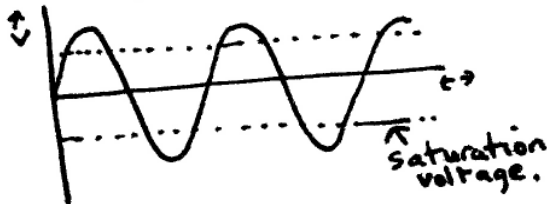

It is like this. Clipping has occurred

